

Applied Fields and Waves  
Project


# Realization of Wilkinson Power Divider

**Group members:**

Aayush Choudhary-2021118

Prince Kumar-2021182

Rohit Barman-2021191

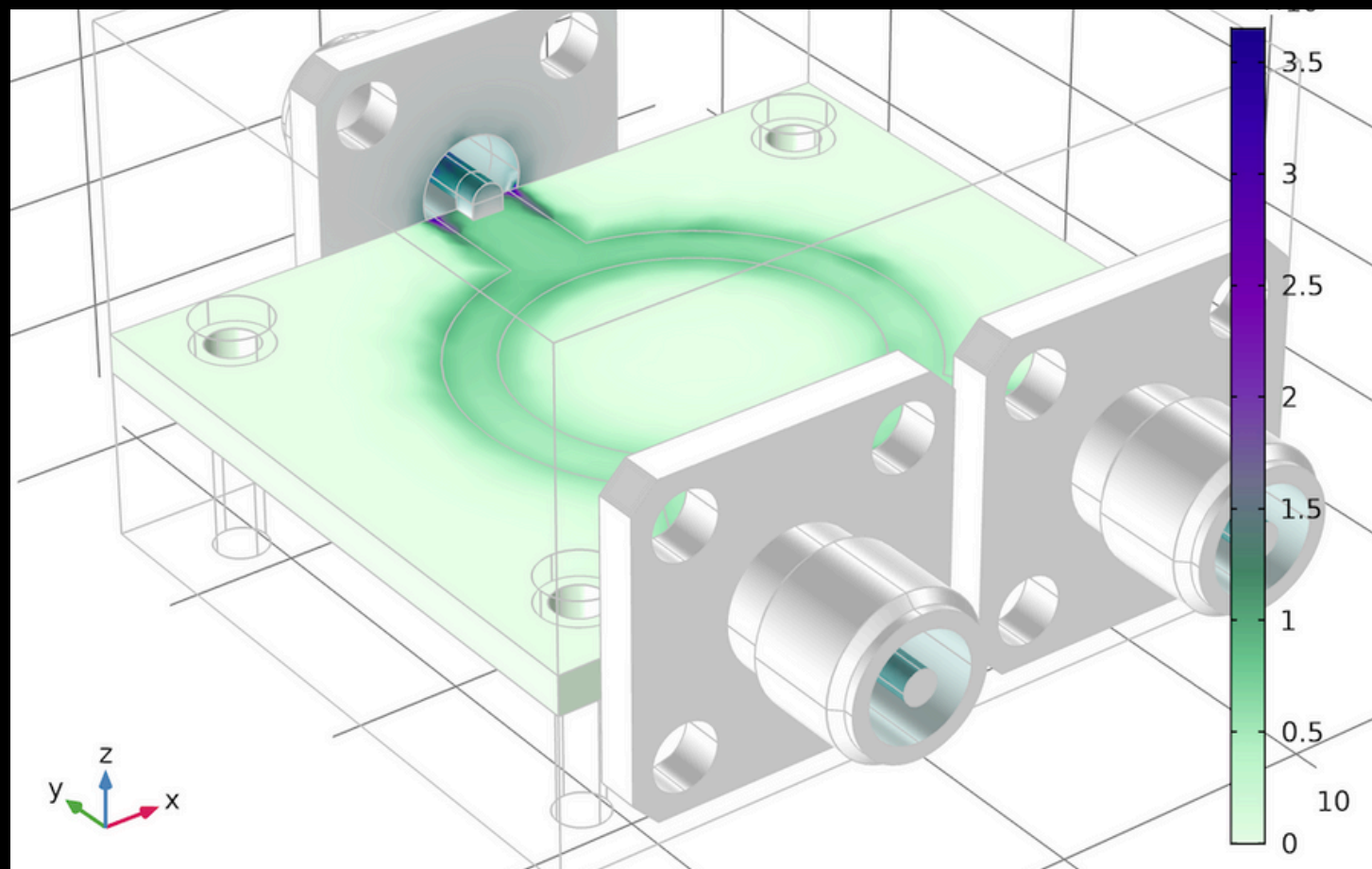


**Instructor : Debidas Kundu**

# Objective and Description

- **Theoretical Analysis:** To study the design principles behind the Wilkinson Power Divider using theoretical models and simulations.
- **Practical Implementation:** To design, simulate, and validate the performance of a Wilkinson Power Divider through full-wave simulation using ADS.
- **Comparison and Optimization:** To compare theoretical predictions with simulation results to identify any discrepancies and optimize the design.

## Description:

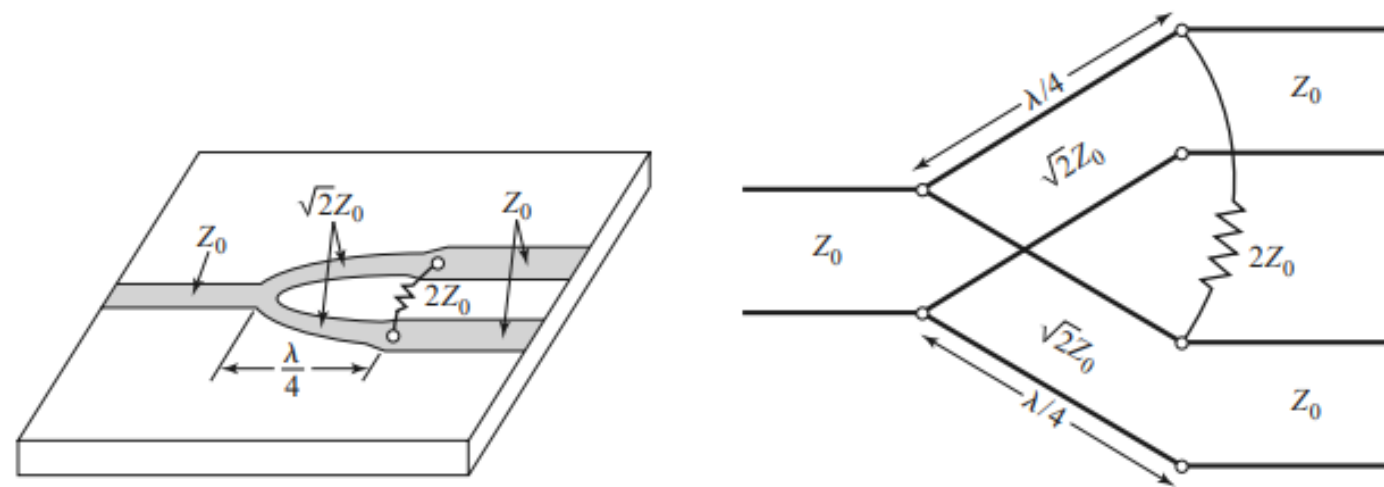

1. A Wilkinson power divider is a passive device used in RF/microwave systems to divide power equally between output ports while maintaining impedance matching.
2. It consists of quarter-wavelength transmission line sections and resistive terminations.
3. It is a 3 port device, i.e., Matched, Reciprocal and Lossy.

# APPROACH

- **Type:** A 3-port device with a distinct scattering matrix.
- **Unique Component:** Features a 2Z0 resistor between ports 2 and 3, enabling both impedance matching at these ports and isolation between them.
- **Resemblance:** Similar to a lossless 3dB divider but enhanced with the resistor for better functionality.

## Design Parameters:

**Frequency :** 1 GHz operation,  
FR4 substrate (H=1.6,  $\epsilon_r=4.4$ , H=1.6  
mm, T=35um, Hu=75 mm( $\lambda/4$ ),  
 $\tan \delta=0.008$ ).


### • Applying Odd/Even Analysis.

#### Even Mode Analysis

- Both Port 2 and Port 3 receive the same voltage, denoted as  $V_{g2}=V_{g3}=2V_0$ .
- Due to this excitation, there is no current flow through the  $r/2$  resistors.
- By bisecting the circuit at these points, the network simplifies, allowing for easier analysis.
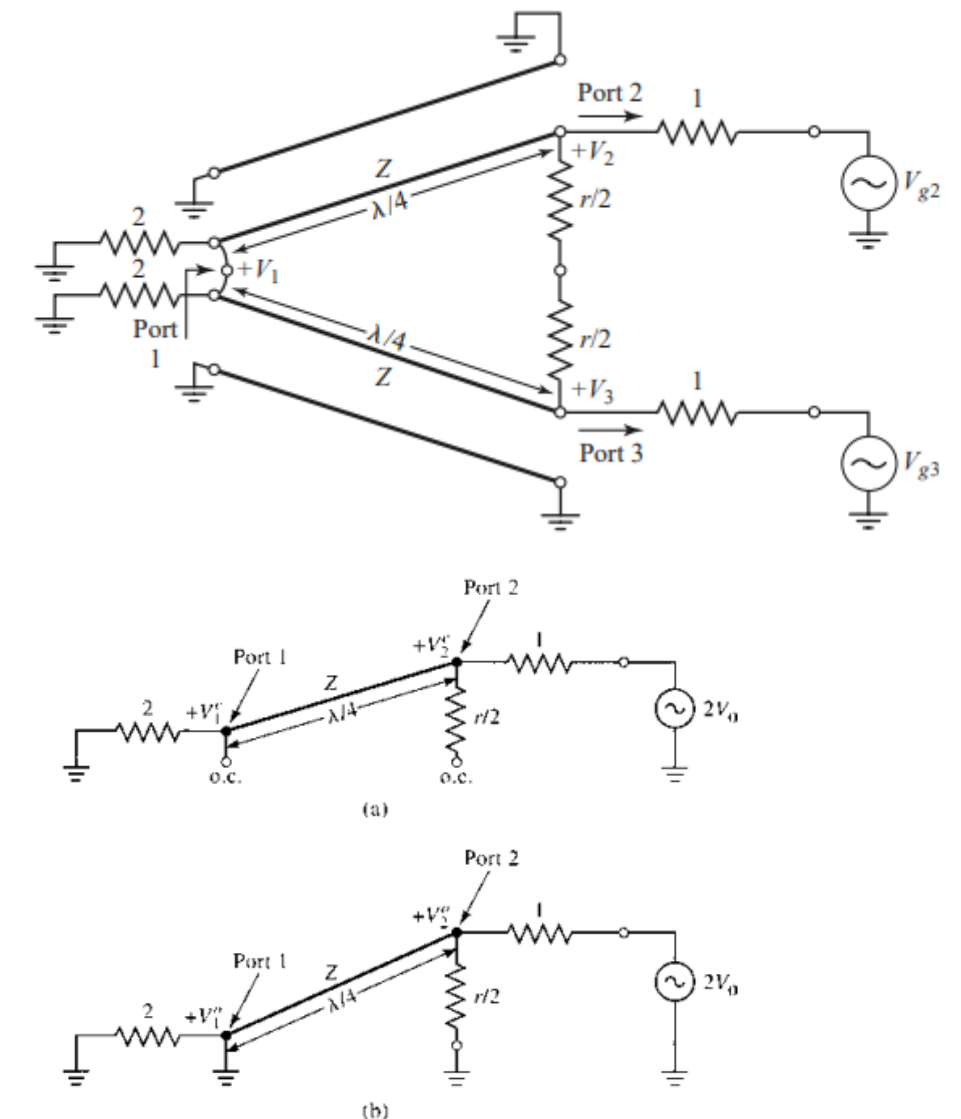
#### Odd Mode Analysis

- In the odd mode, the excitation is such that  $V_{g2}=-V_{g3}=2V_0$ .
- This creates a voltage null along the middle of the circuit.
- Bisecting the circuit under odd mode excitation reveals a different simplified network.



# RESULT

## Impedance Normalization:

- All impedances normalized to the characteristic impedance  $Z_0$ .
- Quarter-wave transmission lines with  $Z = \sqrt{2}Z_0$
- Shunt resistor  $r = 2Z_0$  for isolation and matching.

## Mode Analysis Results:

- **Even Mode:** No current through  $r/2$  resistors; impedance looking into port 2,  $Z_{in} = (Z^2)/2 = 1$ . Effective transmission ensuring matching.
- **Odd Mode:** Voltage null at center; impedance at port 2 seen as open circuit due to  $\lambda/4$  shorted line, confirming isolation.

## Theoretical Predictions

- **Scattering Parameters**

$S_{11} = 0$ : Perfect match at port 1, no reflection.

$S_{22} = S_{33} = 0$ : Ports 2 and 3 are well-matched.

$S_{12} = S_{21} = -j/2^{0.5}$ : Due to the symmetric and reciprocal nature of the network.

$S_{13} = S_{31} = -j/2^{0.5}$ : Symmetry of port 2 and 3.

$S_{23} = S_{32} = 0$ : (due to short or open at bisection).


$$\mathbf{S} = \begin{bmatrix} 0 & -j/\sqrt{2} & -j/\sqrt{2} \\ -j/\sqrt{2} & 0 & 0 \\ -j/\sqrt{2} & 0 & 0 \end{bmatrix}$$

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$$



$$P_2 = (|S_{21}|^2)P_{1+} = P_{1+}/2$$

$$P_3 = (|S_{31}|^2)P_{1+} = P_{1+}/2$$

# SCHEMATIC

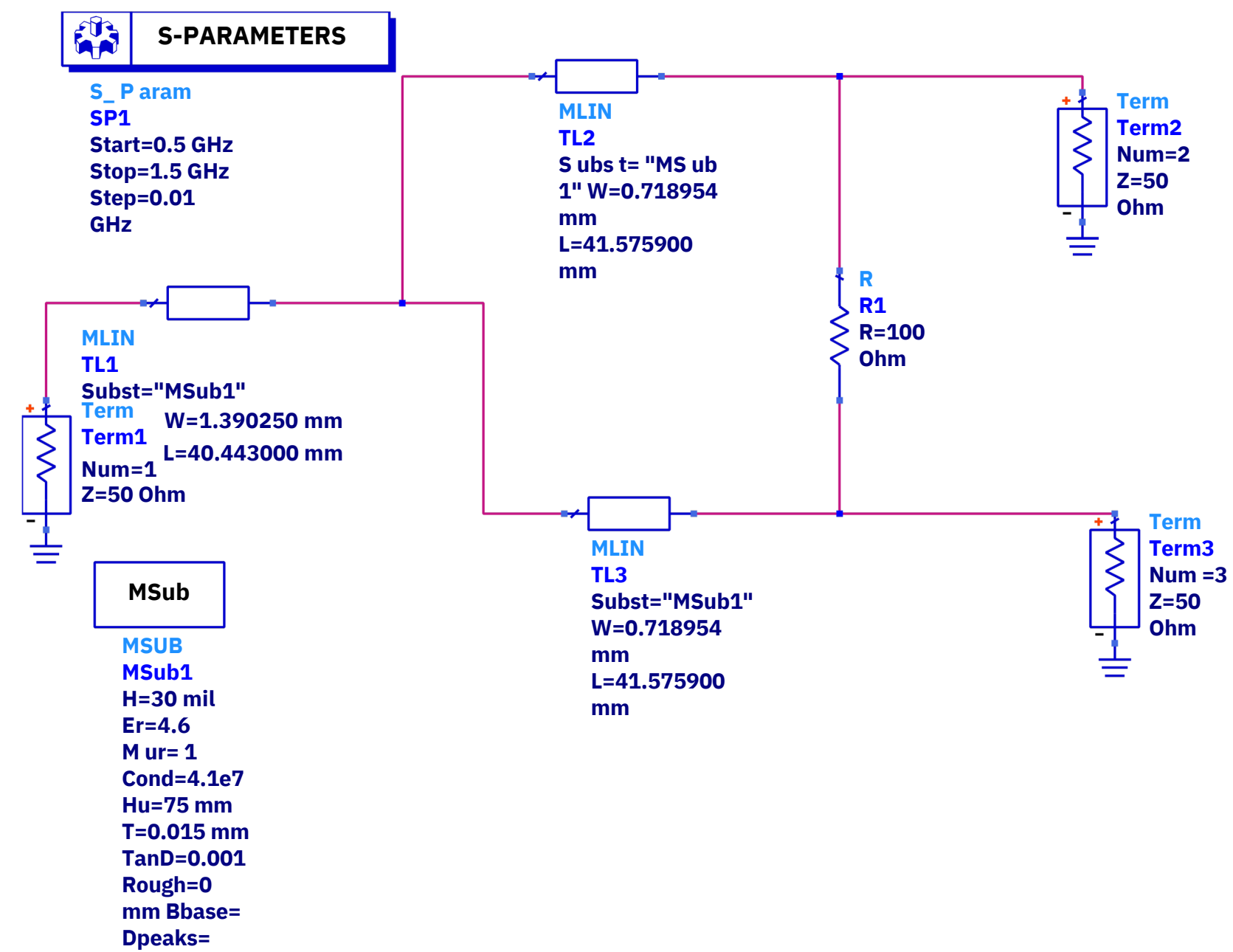

# LAYOUT

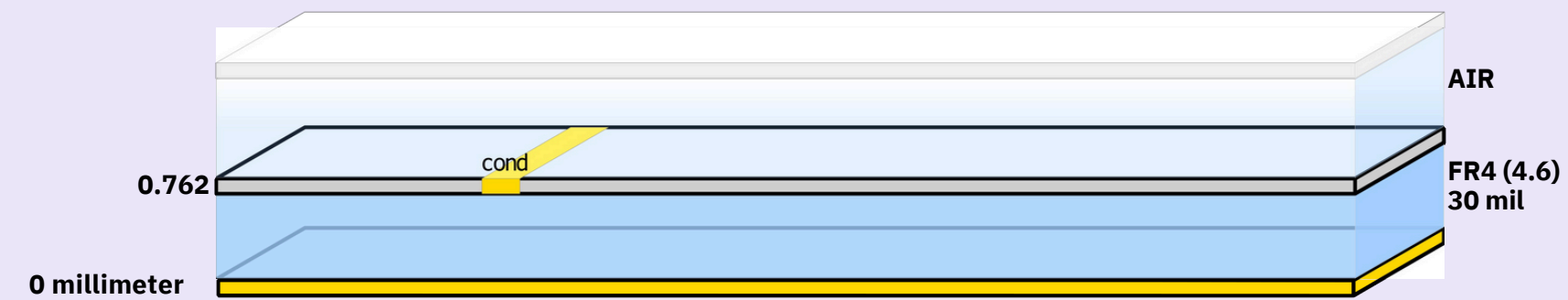
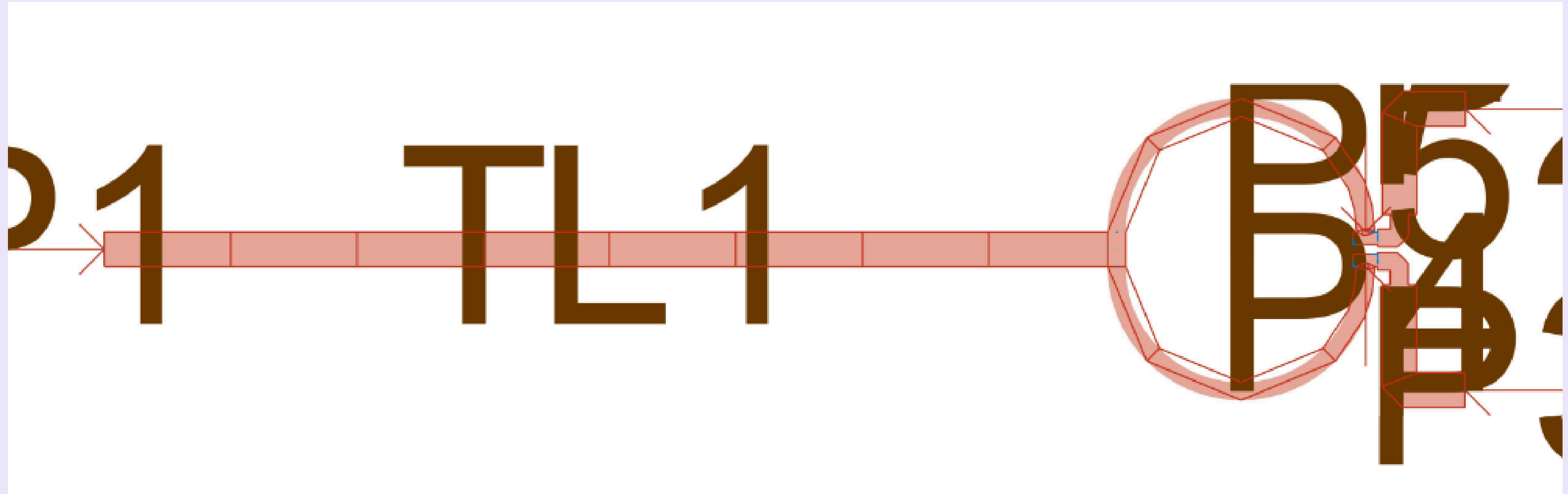


cell\_2 X1

# RESULT
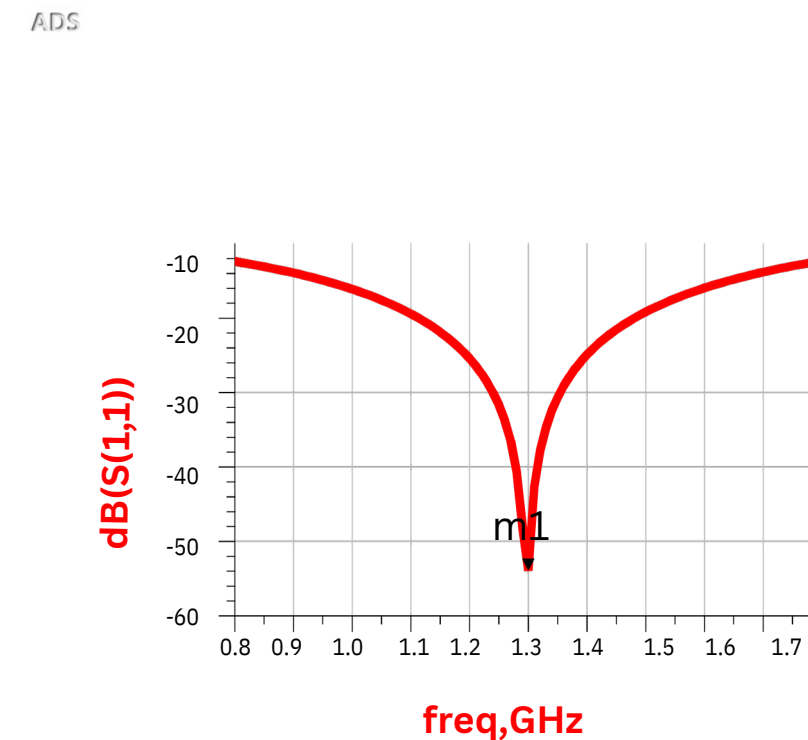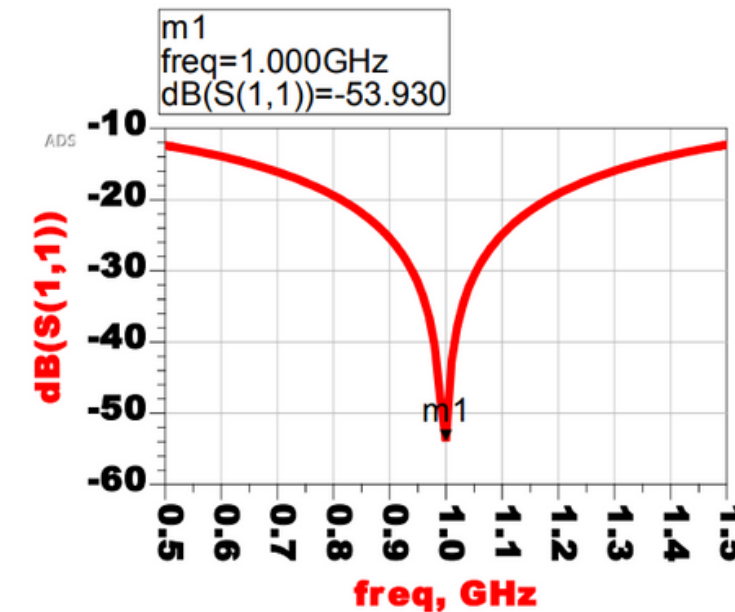
## Empirical Results

- Simulation and Measurement:
- Return loss and insertion loss measured across a frequency range from  $0.5f_0$  to  $1.5f_0$ .
- Matched simulation results with theoretical predictions confirming the design efficacy.
- Highlighted any discrepancies for further analysis.





# PROGRESS AND WORK DISTRIBUTION

## Progress

- **Voltage and S-Parameter Calculations:** Successfully computed node voltages and S-parameters, verifying theoretical predictions.
- **Graphical Results:** Obtained graphs demonstrating the expected performance of the divider.
- **Circuit Design:** Completed both schematic and layout for the Wilkinson Power Divider, ready for simulation.

## Work Distribution

### Prince Kumar:

- Led circuit design and theoretical analysis.
- Prepared simulation data and initial schematics.

### Aayush Choudhary:

- Prepared simulation data and initial schematics..
- Managed data visualization for presentation.

### Rohit Barman:

- Managed project timelines and coordination.
- Handled documentation and presentation materials.



## CONCLUSION

### **Summary of Findings:**

- The Wilkinson Power Divider was thoroughly analyzed and modeled, confirming its capability to split power equally while maintaining excellent impedance matching and isolation between output ports.
- Both theoretical analysis and simulation results demonstrated that the divider operates effectively at the designated frequency with the specified design parameters.

### **Key Achievements:**

- Successful validation of the Wilkinson Power Divider's design through even-odd mode analysis, leading to accurate predictions of its performance.
- Achieved nearly same simulation results and theoretical expectations, underscoring the robustness of the design.

## REFERENCES

- David M. Pozar: Microwave Engineering.
- [https://www.researchgate.net/publication/272986684\\_Design\\_and\\_Realization\\_Wilkinson\\_Power\\_Divider\\_at\\_Frequency\\_2400MHz\\_for\\_Radar\\_S-Band](https://www.researchgate.net/publication/272986684_Design_and_Realization_Wilkinson_Power_Divider_at_Frequency_2400MHz_for_Radar_S-Band)
- [https://youtu.be/CUXAqMJCkb0?si=6x1K-TG\\_Qk3IipN1](https://youtu.be/CUXAqMJCkb0?si=6x1K-TG_Qk3IipN1)

*Thank  
you!*